






Kalisma

29 April 2024

Elektrodinamika

- 1) Hukum Ohm
- 2) Rangkaian Listrik

$$R_1 = 2\Omega$$

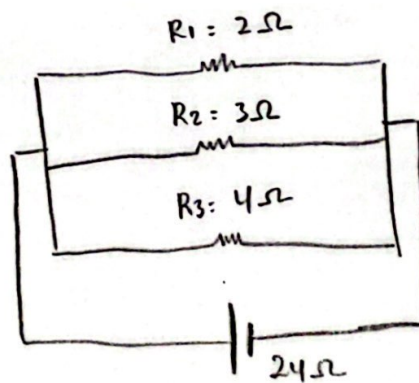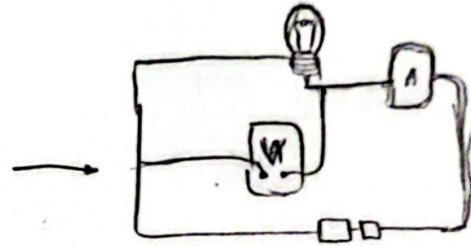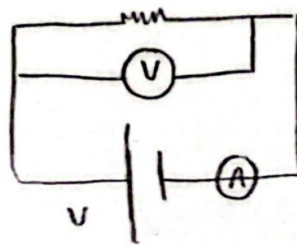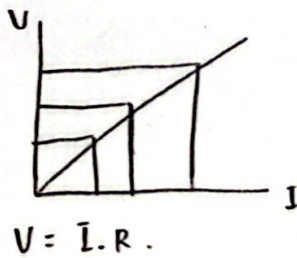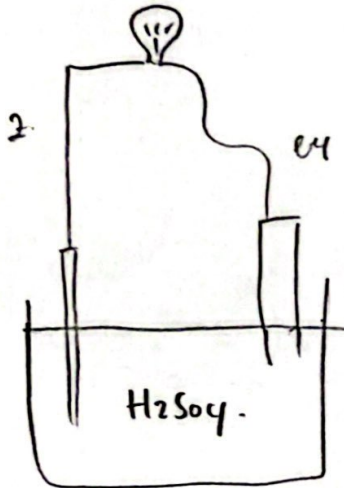


$$R_t = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$



$$\frac{1}{R_t} = \frac{12 + 8 + 6}{24}$$

$$\frac{1}{R_t} = \frac{26}{24}$$

$$R_t = \frac{12}{13}$$
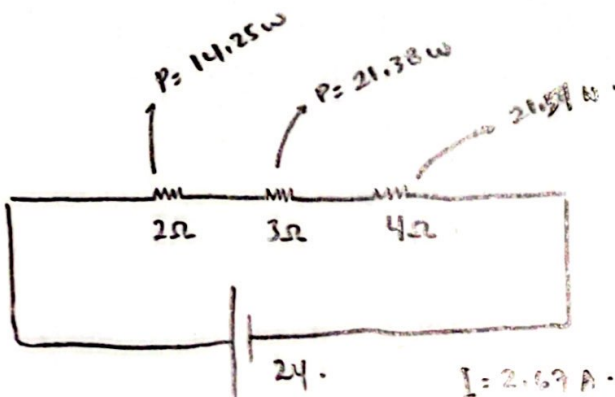
$$I = \frac{V}{R} = \frac{24}{\frac{12}{13}} = 26 \text{ A}$$



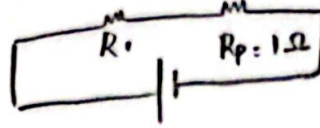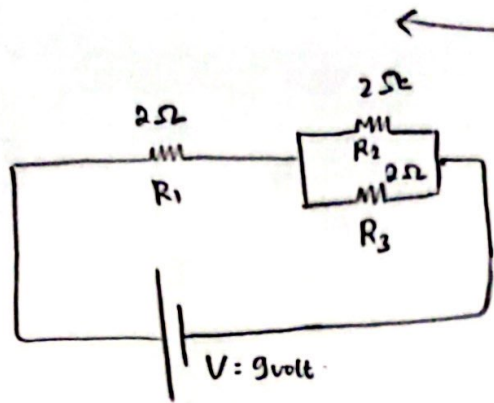

$$R_t = 3\Omega$$


$$I = 3A$$

$$V_{Rp} = I \cdot R_p = 3 \cdot 1 = 3 \text{ volt}$$

$$V_{R2} = 3 \text{ volt}$$

$$V_{R3} = 3 \text{ volt}$$

Hukum Kirchhoff

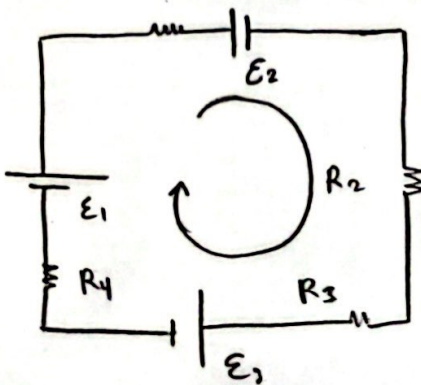


$$E_1 > E_2 > E_3$$

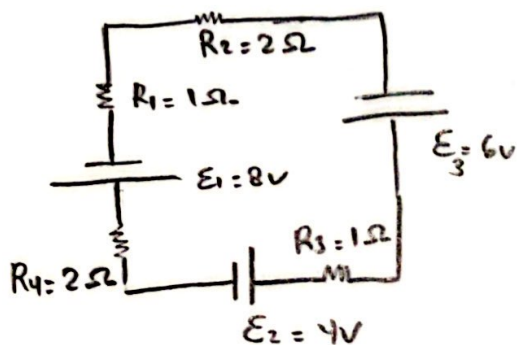- 1) Gambar arah arus sesuai dengan besarnya.
- 2) Gambar loop
- 3) Jika arah arus searah dengan arah loop, maka +.

$$\sum E + \sum I \cdot R = 0$$

$$\hookrightarrow E_1 + E_2 + E_3 + I(R_1 + R_2 + R_3) = 0$$



$$\sum E + \sum IR = 0$$

$$E_1 + E_2 - E_3 - I(R_1 + R_2 + R_3 + R_4) = 0$$

$$8 + 4 - 6 - I(1 + 2 + 1 + 2) = 0$$

$$6 - I(6) = 0$$

$$I = \frac{6}{6}$$

$$I = 1A, \text{ jadi, arus yang mengalir adalah } 1A.$$