

Kalisma.

Elektrodinamika






1. hukum Ohm

2. Rangkaian listrik.

Pembahasan


$$J = \sigma E \quad \text{DC}$$

$$V = I R \quad \text{AC}$$

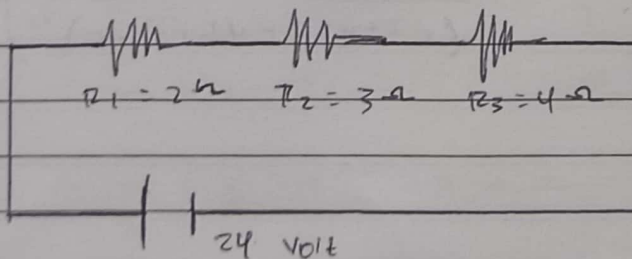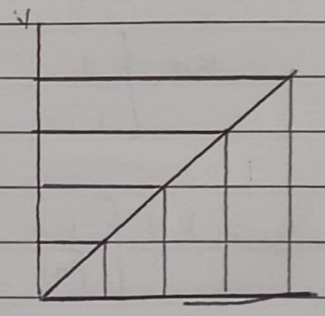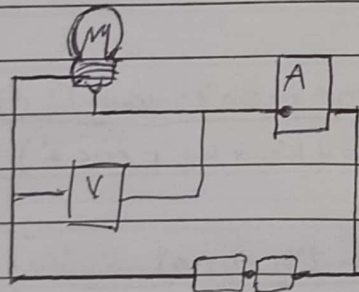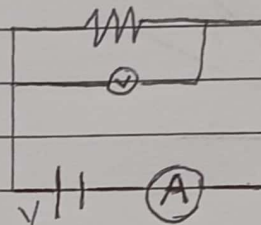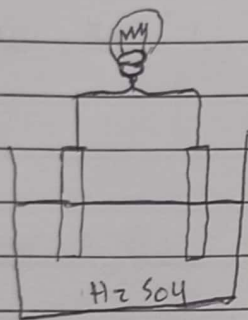

$$R_t = 9\Omega$$

$$I = \frac{27}{9} = 3\text{ A}$$

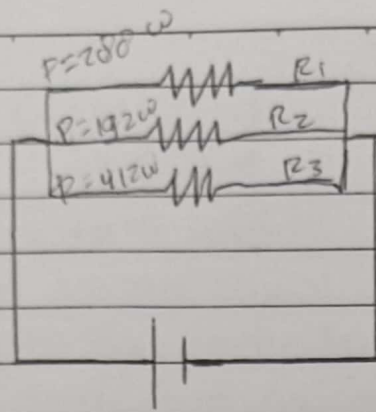

$$R_1 = 2 \Omega$$

$$R_2 = 3 \Omega$$

$$R_3 = 4 \Omega$$

$$R_t = \frac{1}{\frac{1}{R_t}} = \frac{1}{\frac{1}{2} + \frac{1}{3} + \frac{1}{4}}$$

$$\frac{1}{R} = \frac{12 + 8 + 6}{24}$$



$$\frac{1}{R_t} = \frac{26}{24}$$

$$R_t = \frac{12}{13}$$

$$I = \frac{V}{R}$$

$$= 24 \frac{13}{12}$$

$$= 26 \text{ A.}$$

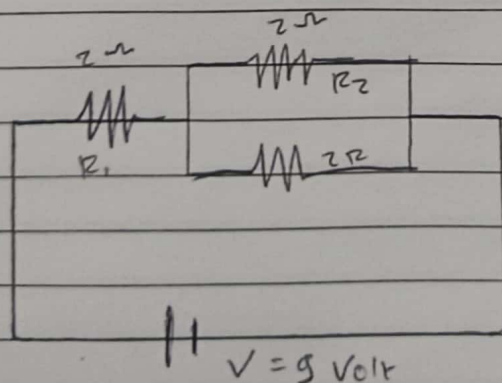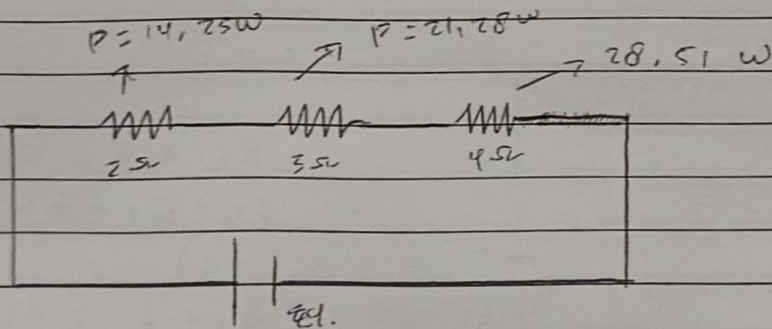

$$R_t = 3 \Omega$$


$$I = 3 \text{ A}$$

$$V_{R1} = I \cdot R_1 = 3 \cdot 1 = 3 \text{ volt}$$

$$V_{R2} = 3 \text{ volt}$$

$$V_{R3} = 3 \text{ volt}$$

$$V = 9 \text{ Volt}$$

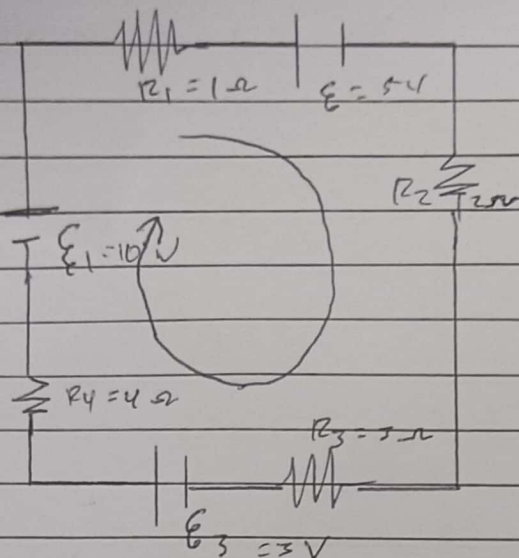

$$\mathcal{E}_1 > \mathcal{E}_2 > \mathcal{E}_3$$

1. Gambar arah arus sesuai dengan besarnya $\mathcal{E}$
2. Gambar lup sesuai hati
3. jika arah arus searah dengan arah loop maka +


$$= -10 + 5 + 3 + I(1 + 2 + 3 + 4) = 0$$

$$= -2 + I(10) = 0$$

$$I(10) = 2$$

$$I = \frac{2}{10}$$

$$I = 0,2 \text{ A.}$$

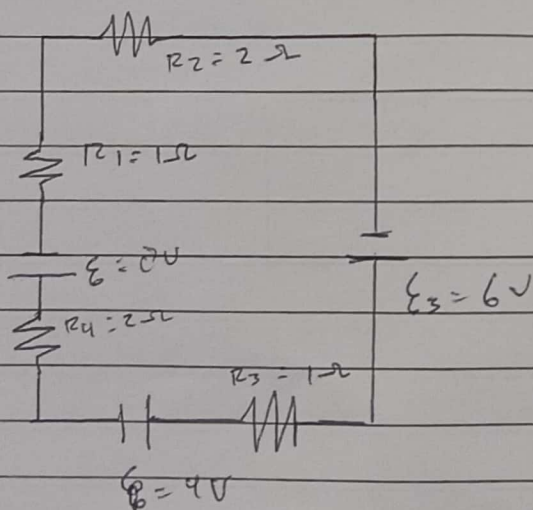

$$\sum \mathcal{E} + \sum I \cdot R = 0$$


$$\mathcal{E}_1 + \mathcal{E}_2 - \mathcal{E}_3 - I(R_1 + R_2 + R_3 + R_4) = 0$$

$$8 + 4 - 6 - I(1 + 2 + 1 + 2) = 0$$

$$6 - I(6) = 0$$

$$I = \frac{6}{6}$$

$$= 1 \text{ A.}$$

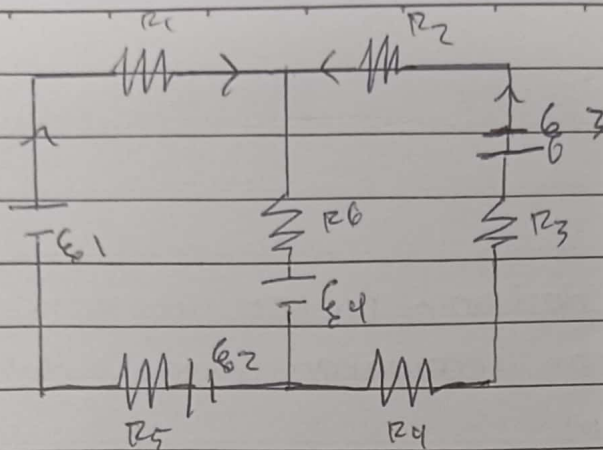

loop 1

$$\sum E + \sum I \cdot R = 0$$

$$-E_1 + E_4 + E_2 + I_1(R_1 + R_5) +$$

$$I_3 R_6 = 0$$

loop 2

$$\sum E + \sum I \cdot R = 0$$

$$-E_3 + E_4 + I_2(R_2 + R_3 + R_4) + I_3 R_6 = 0$$