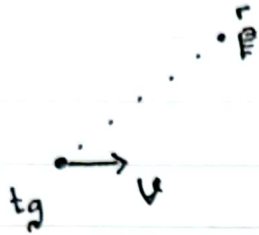


Kalisma

MEDAN MAGNET


1. Medan magnet oleh muatan bergerak.




$$\vec{B} = \frac{\mu_0 q v \times \hat{r}}{4\pi r^2}$$

$$= \frac{\mu_0 q v}{4\pi r^2} \sin \theta$$

2. $\vec{B}$ oleh arus listrik



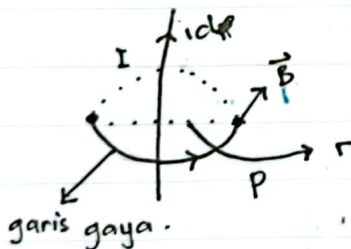

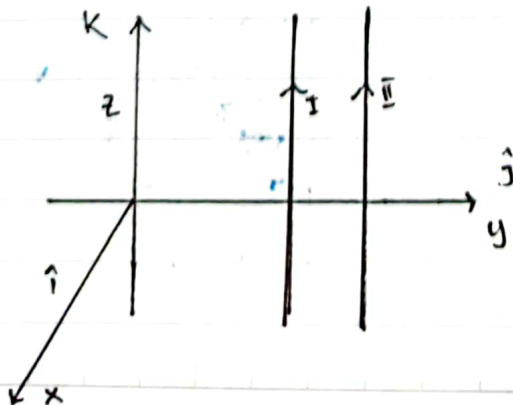
$$\vec{B} = \frac{\mu_0}{4\pi} \frac{I d\vec{l} \times \hat{r}_0}{r^2}$$







$$\vec{B} = \frac{\mu_0}{4\pi} \frac{I d\vec{l} \times \hat{r}}{r^2}$$
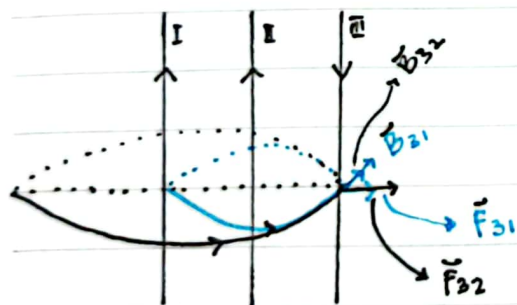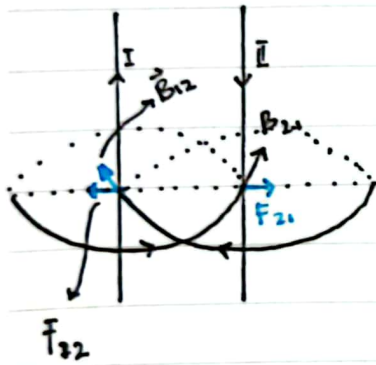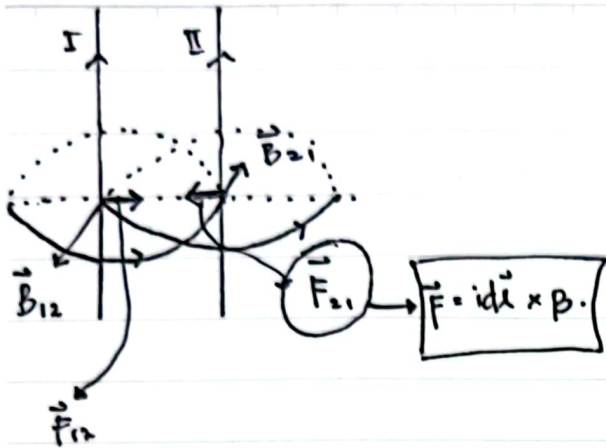
$$= \frac{\mu_0}{4\pi} \frac{I d\vec{l}}{r^2} \sin \theta (-\hat{r})$$



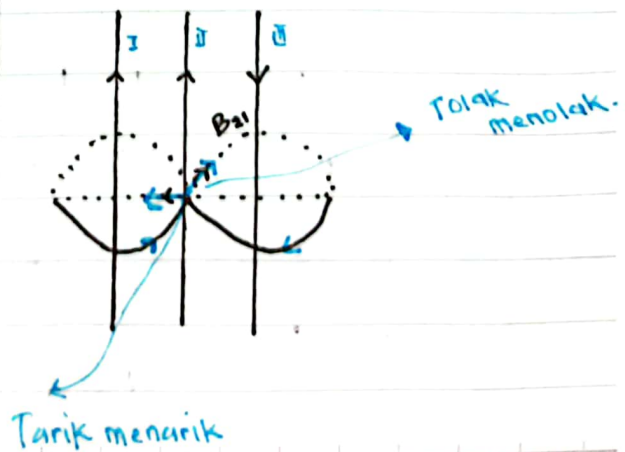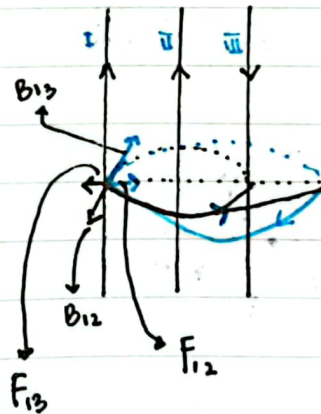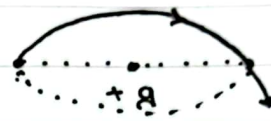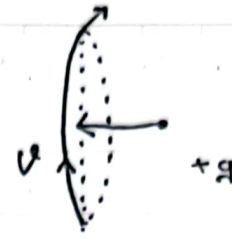
Medan magnet selalu menyilang garis gaya.



Npm : 2213021009 / A

75

1.

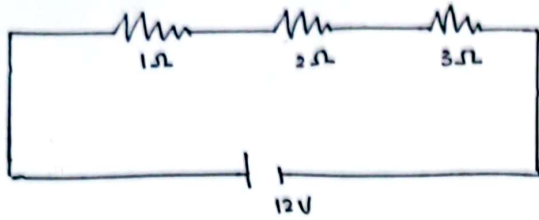

- Hitung arus pada R_3
- Hitung tegangan pada R_2 .

Jawab:

$$a). I_{R_3} = \frac{V}{R_{total}}$$

$$= \frac{12}{1\Omega + 2\Omega + 3\Omega}$$

25

$$= \frac{12}{6}$$

$$= 2 \text{ A}$$

$$\begin{aligned} b). V &= R \cdot I \\ &= 2 \times 2 \\ &= \frac{12 \cdot V}{3} \\ &= 4 \text{ V} \end{aligned}$$

$$\begin{aligned} \rightarrow I_{R_2} &= \frac{V}{R_2} \\ &= \frac{12}{62} \\ &= 6 \text{ A} \end{aligned}$$

Jawab:

$$R_{total} = \frac{1}{\frac{1}{1} + \frac{1}{2} + \frac{1}{3}}$$

$$= \frac{6 + 3 + 2}{6} = \frac{11}{6} = 1.83 \Omega$$

$$I_{R_3} = \frac{V}{R}$$

$$= \frac{12}{1.83}$$

$$= 6.55 \text{ A}$$

15

$$b). \text{ Tegangan } \begin{matrix} R_1 \\ R_2 \\ R_3 \end{matrix} \left. \vphantom{\begin{matrix} R_1 \\ R_2 \\ R_3 \end{matrix}} \right\} 12 \text{ V}$$


Tegangan R_2

$$V_{R_2} = I \times R$$


$$= 12 \times 1.83$$

$$= 21.96 \text{ V}$$

2.

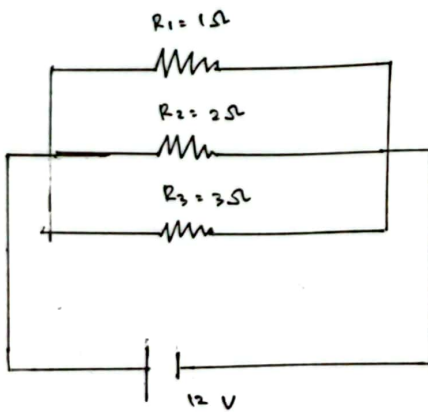

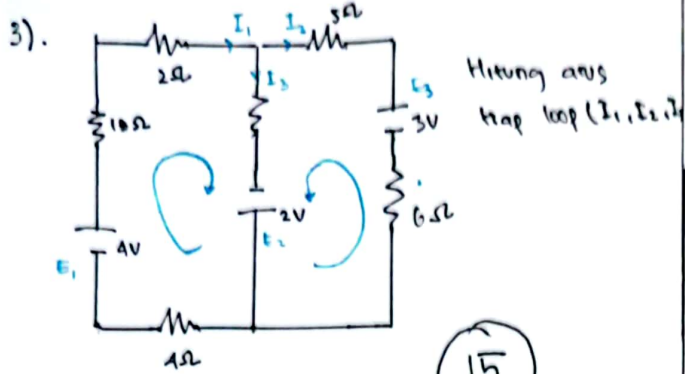- Hitung arus pada R_3
- Hitung tegangan pada R_2



Jawab:
diket:

$$\begin{array}{lll} E_1 = 4V & R_1 = 1\Omega & R_5 = 5\Omega \\ E_2 = 2V & R_2 = 2\Omega & R_6 = 6\Omega \\ E_3 = 3V & R_3 = 3\Omega & \\ & R_4 = 1\Omega & \end{array}$$

Loop I_1

$$\sum E + \sum IR = 0$$

$$-E_1 + E_2 + I_1(R_1 + R_2 + R_4) + I_3(R_3) = 0$$

$$-4 + 2 + I_1(1 + 2 + 1) + I_3(3) = 0$$

$$-2 + I_1(4) + I_3(3) = 0$$

$$-2 + I_1(10) = 0$$

$$I_1(10) = 2$$

$$I_1 = \frac{2}{10}$$

$$I_1 = 0.2 \text{ A}$$

loop I_2

$$\sum E + \sum IR = 0$$

$$-E_3 + E_2 + I_2(R_5 + R_6) + I_3(R_3) = 0$$

$$-3 + 2 + I_2(5 + 6) + I_3(3) = 0$$

$$-1 + I_2(11) + I_3(3) = 0$$

$$-1 + I_2(14) = 0$$

$$I_2(14) = 1$$

$$I_2 = \frac{1}{14}$$

$$I_2 = 0.07 \text{ A}$$

Arus loop 1 dan 2 adalah 0.2 A dan 0.07 A.

4.

