


- a. hitung arus pada R3
b. hitung tegangan pada R2

Jawab

a) $\frac{12}{6} = 2 \text{ A}$ b) $\frac{12}{3} = 4$

25

B: 80

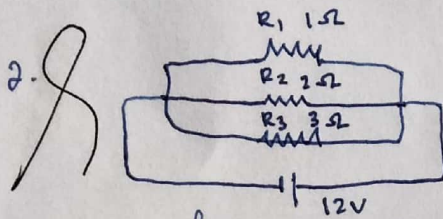


- a. hitung arus R3
b. hitung tegangan R2

Jawab:

a. $\frac{12}{3} = 4 \rightarrow R3$
b. $\frac{12}{2} = 6 \rightarrow R2$

$\left\{ \begin{array}{l} 12 : 1 = 12 \\ 12 : 2 = 6 \\ 12 : 3 = 4 \end{array} \right.$

15

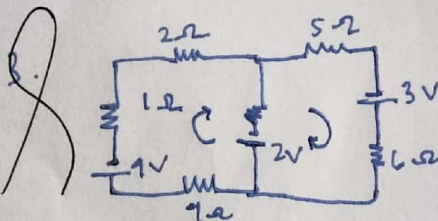

hitung arus tiap loop (I_1, I_2, I_3)

Jawab:


$\sum \xi + \sum I \cdot R = 0$
 $-1 - 2 + I_1 + 3I_3 = 0$
 $-6 + 2I_1 + 3I_3 = 0$

loop I

$\sum \xi + \sum I \cdot R = 0$
 $-2 + \xi_3 + I_2 + I_3 = 0$
 $R6 = 0 \quad 11 - I(11) = 0$
 $I = \frac{11}{11} = 1 \text{ A}$

loop II

15

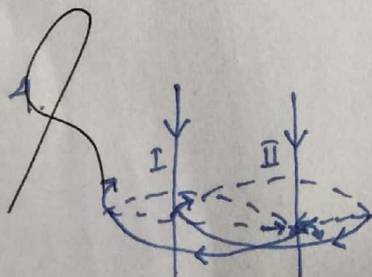

25