

Usaha dan Energi



$$W = -q \left[-\frac{q}{4\pi\epsilon_0 r} \right]$$

$$= q[V]$$


$$W = qV$$

$$W = \int_A^B \vec{F} \cdot d\vec{L}$$

$$= -q \int E dr$$

$$= -q \left[\int \frac{1}{4\pi\epsilon_0} \frac{q}{r^2} dr \right]$$

Contoh hal: 13

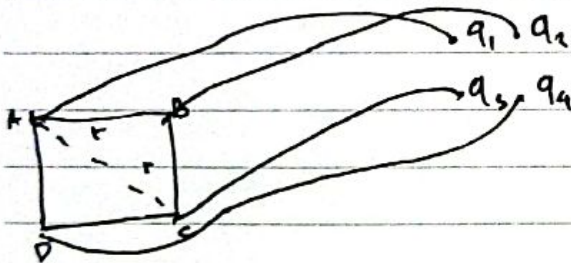

$$W_1 = q_1 \cdot V_1 = 0$$

$$W_2 = q_2 \cdot V_2 = q_2 \left[k \frac{q_1}{r_1} \right]$$

$$W_2 = q_2 \cdot V_2$$

$$W_3 = q_3 V_3$$

$$= q_3 \left[k \frac{q_1}{r_1} + k \frac{q_2}{r_2} \right]$$

$$= q_3 \left[\dots \right]$$

$$W_4 = q_4 V_4 = q_4 \left[k \frac{q_1}{r_1} + k \frac{q_2}{r_2} + k \frac{q_3}{r_3} \right]$$

$$W_k = W_1 + W_2 + W_3 + W_4$$

$$= k \frac{q_1 q_2}{r_1} + k \frac{q_1 q_3}{r_1} + k \frac{q_2 q_3}{r_2} + \dots$$

$$W = \frac{1}{4\pi\epsilon_0} \sum_{i=1}^n \sum_{j=1, j \neq i}^n \frac{q_i q_j}{r_{ij}}$$

$$W = \frac{1}{2} \sum_{i=1}^n q_i v_i$$

$$W = \frac{1}{2} \int \lambda v dl$$

$$W = \frac{1}{2} \int \sigma v ds$$

$$W = \frac{1}{2} \int \rho v dG$$


$$\rho = \epsilon_0 (\nabla \cdot \vec{E})$$

$$\nabla \cdot \vec{E} = \frac{\rho}{\epsilon_0}$$

$$W = \frac{\epsilon_0}{2} \int E^2 d\tau$$



• Metode bayangan

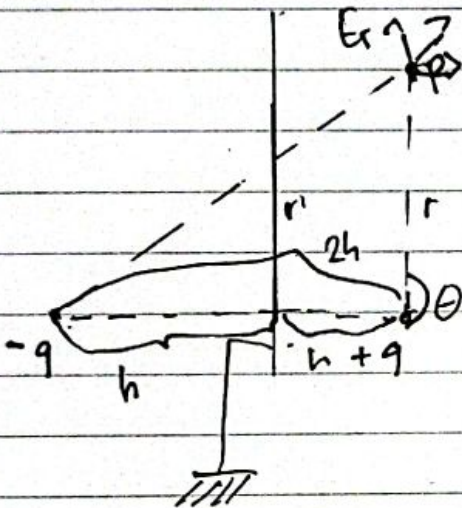

$$V = \frac{1}{4\pi\epsilon_0} \frac{q}{r} + \frac{1}{4\pi\epsilon_0} \frac{-q}{r'}$$

$$V = \frac{q}{4\pi\epsilon_0} \left[\frac{1}{r} - \frac{1}{r'} \right] \quad r' = (r^2 + 4h^2 + 4hr \cos \theta)^{\frac{1}{2}}$$

$$E_r = \frac{dV}{dr} = K \left[\frac{1}{r^2} - \frac{1}{(r^2 + 4h^2 + 4hr \cos \theta)^{\frac{3}{2}}} (2r + 4h \cos \theta) \right]$$


$$= K \left[\frac{1}{r^2} - \frac{(2r + 4h \cos \theta)}{(r^2 + 4h^2 + 4hr \cos \theta)^{\frac{3}{2}}} \right]$$

Elektrodinamika

> Hukum Ohm


> Rangkaian Listrik
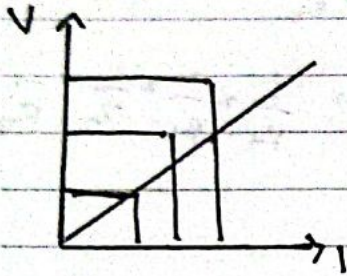
$$V = I \cdot R \rightarrow \text{tetap}$$



Arus dirangkai seri itu sama

$$I = I_{R_1} = I_{R_2} = I_{R_3}$$

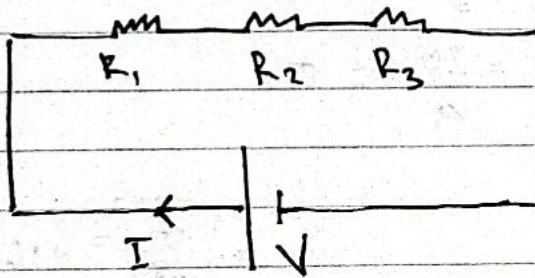

$$\begin{aligned} I_{R_1} &= \frac{V}{(R_1 + R_2 + R_3)} \\ &= \frac{V}{R_t} \\ I_{R_2} &= \frac{V}{R_t} \\ I_{R_3} &= \frac{V}{R_t} \end{aligned}$$


$$V_{R_1} = I \cdot R_1$$

$$V_{R_1} = \frac{V}{(R_1 + R_2 + R_3)} \cdot R_1$$

$$V_{R_2} = \frac{V}{(R_1 + R_2 + R_3)} \cdot R_2$$

$$V_{R_3} = \frac{V}{(R_1 + R_2 + R_3)} \cdot R_3$$

$$I = \frac{V}{(R_1 + R_2 + R_3)}$$

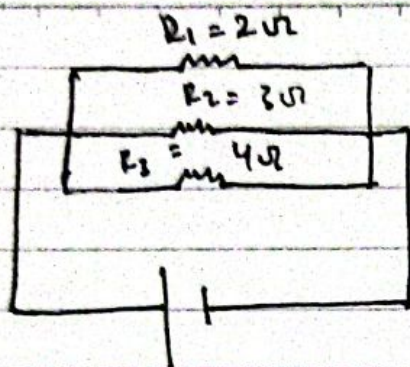

$$V = 20V$$

$$V_{R1} = V_{R2} = V_{R3} = V$$

$$I_{R1} = \frac{V}{R_1}$$

$$I = \frac{V}{R_t}$$

$$I_{R2} = \frac{V}{R_2}$$

$$R_t? \quad \frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I_{R3} = \frac{V}{R_3}$$

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I_{R1} = \frac{20}{2} = 10$$

$$= \frac{1}{2\Omega} + \frac{1}{3\Omega} + \frac{1}{4\Omega}$$

$$I_{R2} = \frac{20}{3} = 6.6$$

$$= \frac{6 + 4 + 3}{12}$$

$$I_{R3} = \frac{20}{4} = 5$$

$$= \frac{13}{12}$$

$$3 \sqrt{\frac{20}{18}} = 6.6$$


$$R_t = \frac{12}{13} = 0.92$$

$$I = \frac{V}{R_t}$$

$$= \frac{20}{0.92} \Rightarrow \frac{20}{\frac{12}{13}} = 20 \cdot \frac{13}{12}$$

$$= 21.73 A$$

$$= 21.67 A$$

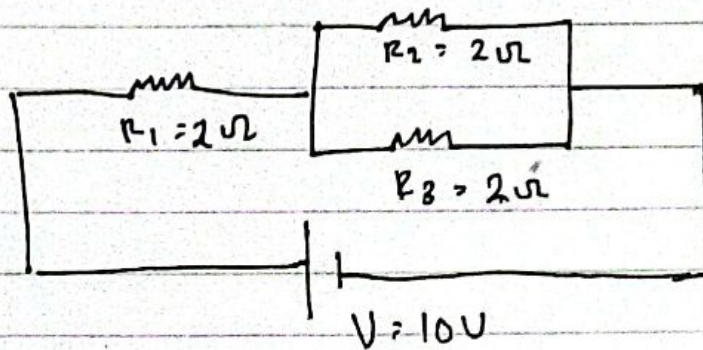

$$\frac{1}{R_{tp}} = \frac{1}{R_2} + \frac{1}{R_3} \quad I_{R2} = I_{R3} = \frac{V_{R2}}{R_2}$$

$$= \frac{1}{2} + \frac{1}{2} \quad = \frac{3.33}{2}$$

$$= 1 \quad = 1.66 A$$

$$R_t = R_1 + R_{tp}$$

$$= 2 + 1$$

$$= 3$$

$$V_{R1} = \frac{V}{R_t} \cdot R_1 = \frac{10}{3} \cdot 2 = 3.33 \cdot 2$$

$$= 6.66 V$$

$$I_t = \frac{V}{R_t} = \frac{10}{3} = 3.33 A$$

$$I_R = 3.33 A$$

$$I_{R2} = 3.33 \rightarrow V_{R2} = R_2 \cdot I = 1 \cdot 3.33$$

$$= 3.3 \text{ Volt}$$

$$L_2 = L_3 < L_1$$