

# **Lecture 3**

## **Processor: Datapath and Control**

# ALU


- Arithmetic Logic Unit is the hardware that performs addition, subtraction, AND, OR ...

# Recap: Performance

$\text{CPU Time} = \text{Instruction Count} \times \text{CPI} \times \text{Clock Cycle Time}$

- CPU performance factors
  - Instruction count
    - Determined by Instruction Set Architecture and compiler
  - CPI and Cycle time
    - Determined by implementation of the processor

# Components of a Computer

 

# Processor

- Datapath


- Components of the processor that perform arithmetic operations and holds data

- Control


- Component of the processor that commands the datapath, memory, I/O devices according to the instructions of the memory
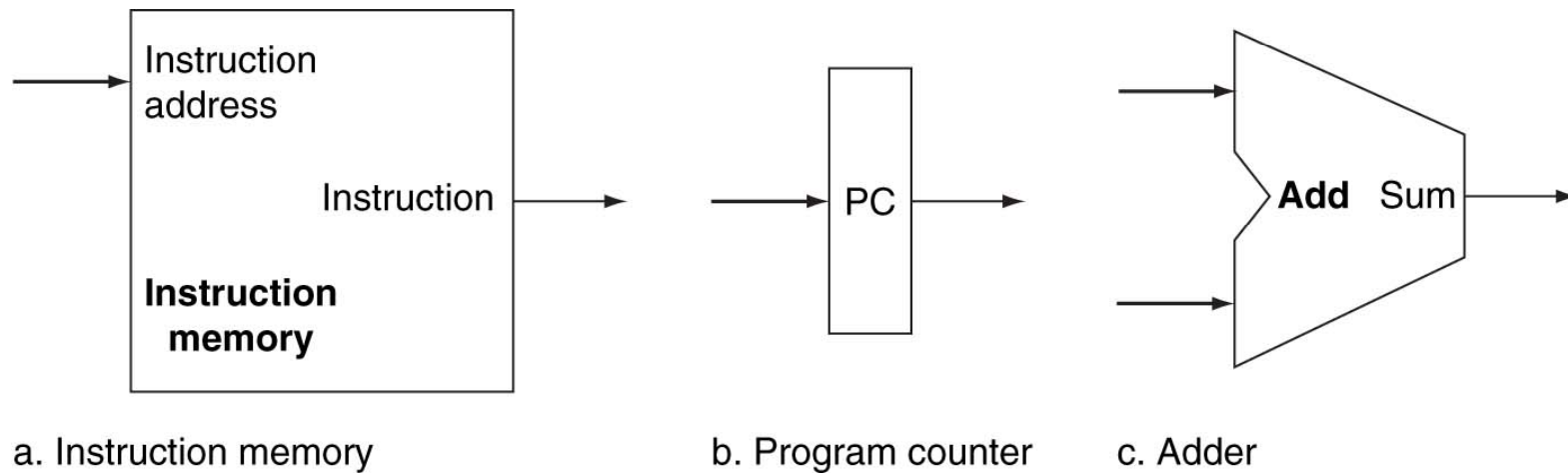
# Building a Datapath

- Datapath
  - Elements that process data and addresses in the CPU
    - Memories, registers, ALUs, ...
- We will build a MIPS datapath incrementally
  - considering only a subset of instructions
- To start, we will look at 3 elements




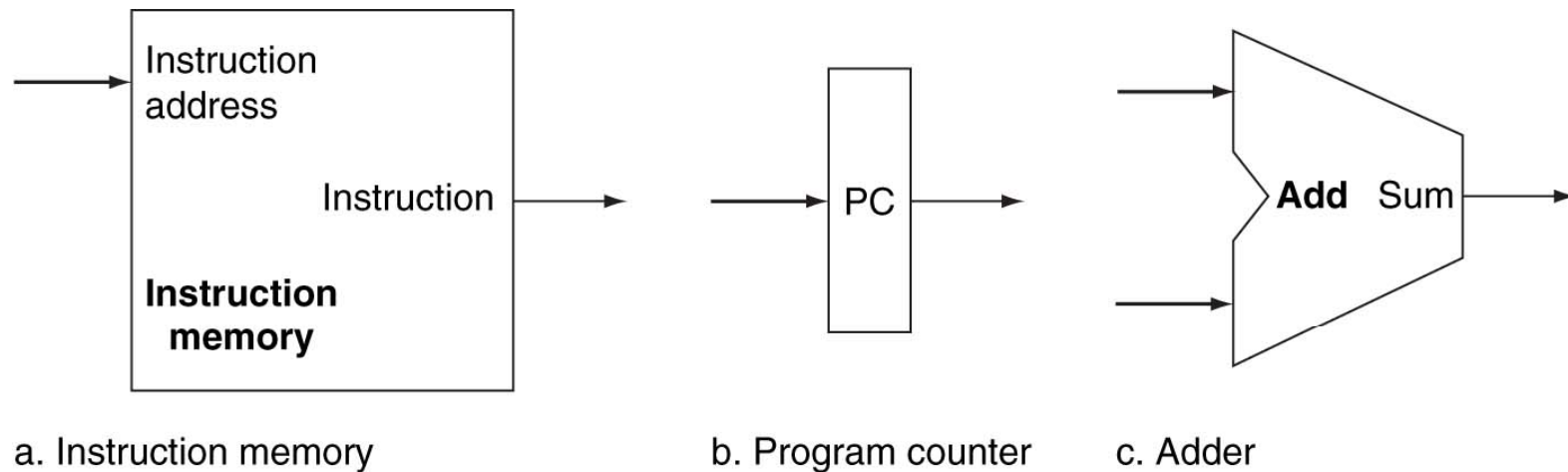- A memory unit to store instructions of a program and supply instructions given an address
- Needs to provide only read access (once the program is loaded).
  - No control signal is need.



 
- PC (Program Counter or Instruction address register) is a register that holds the address of the current instruction
- A new value is written to it every clock cycle. No control signal is required to enable write





- Adder to increment the PC to the address of the next instruction
- An ALU permanently wired to do only addition. No extra control signal required

# Datapath portion for Instruction Fetch

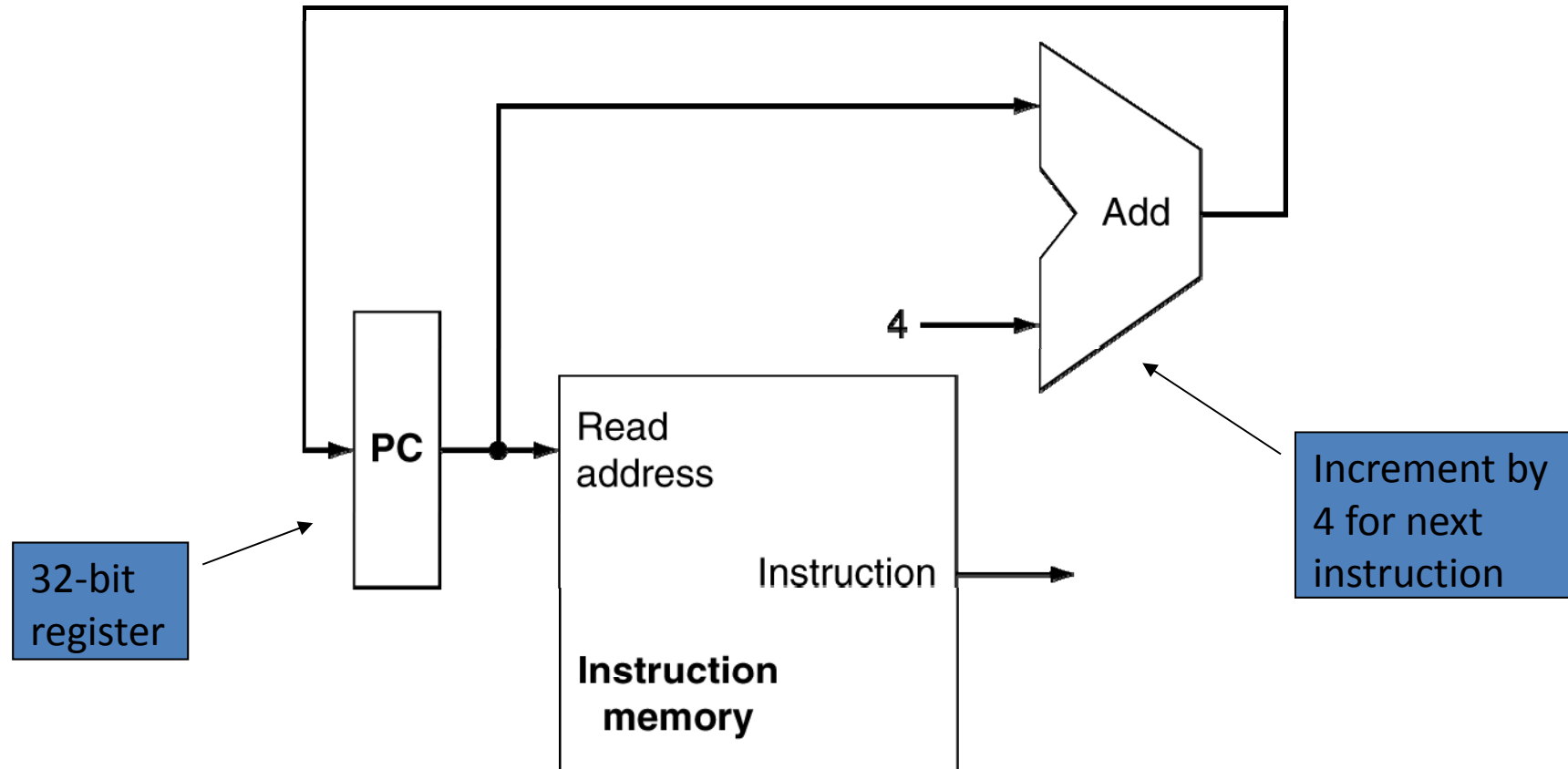

# Types of Elements in the Datapath


- State element:
  - A memory element, i.e., it contains a state
  - E.g., program counter, instruction memory
- Combinational element:
  - Elements that operate on values
  - E.g. adder, ALU

- Now, we will look at datapath elements required by the different classes of instructions
  - Arithmetic and logical instructions
  - Data transfer instructions
  - Branch instructions


# R-Format ALU Instructions

- E.g., ***add \$t1, \$t2, \$t3***
- Perform arithmetic/logical operation
- Read two register operands and write register result


# R-Format ALU Instructions

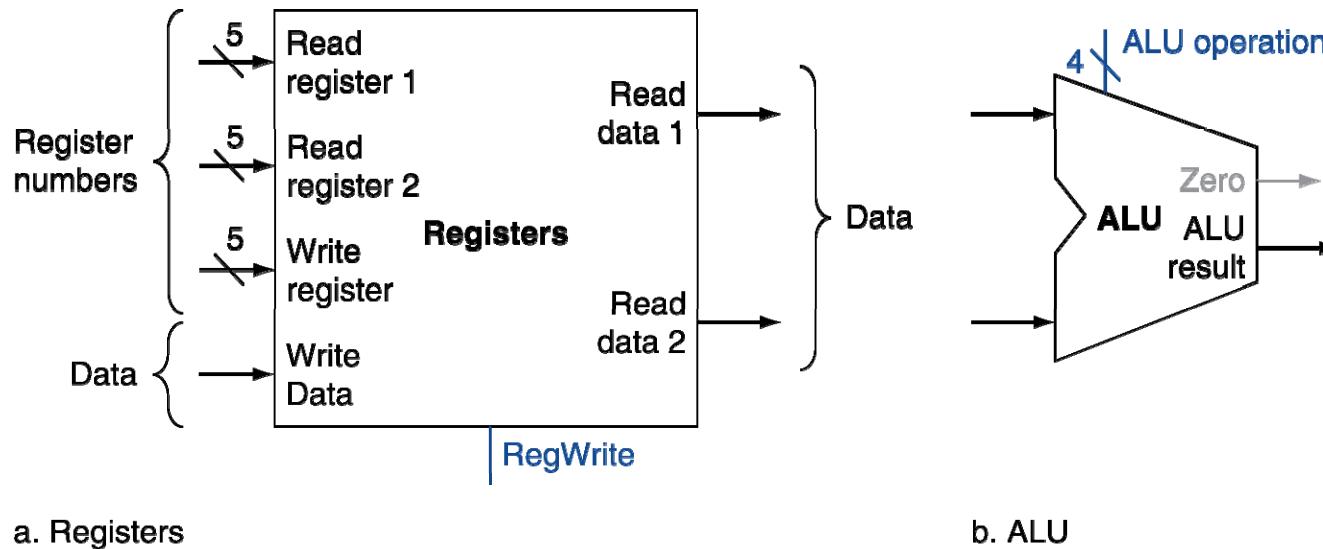

 - Register file: A collection of the registers
  - Any register can be read or written by specifying the number of the register
  - Contains the register state of the computer




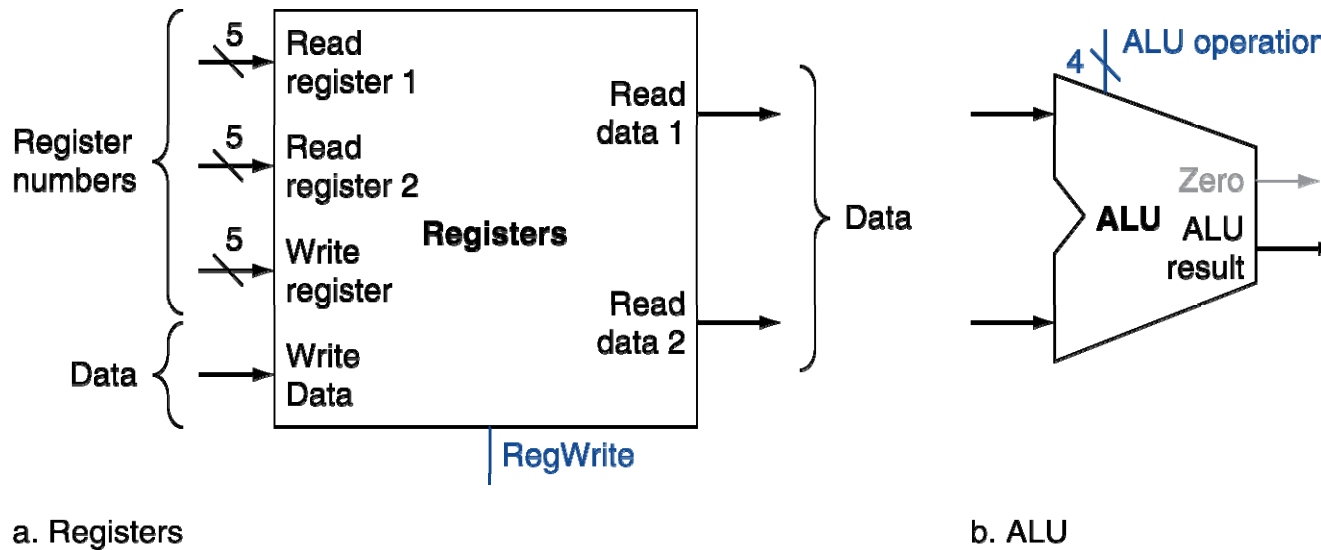- Read from register file
  - 2 inputs to the register file specifying the numbers
    - 5 bit wide inputs for the 32 registers
  - 2 outputs from the register file with the read values
    - 32 bit wide
  - For all instructions. No control required.



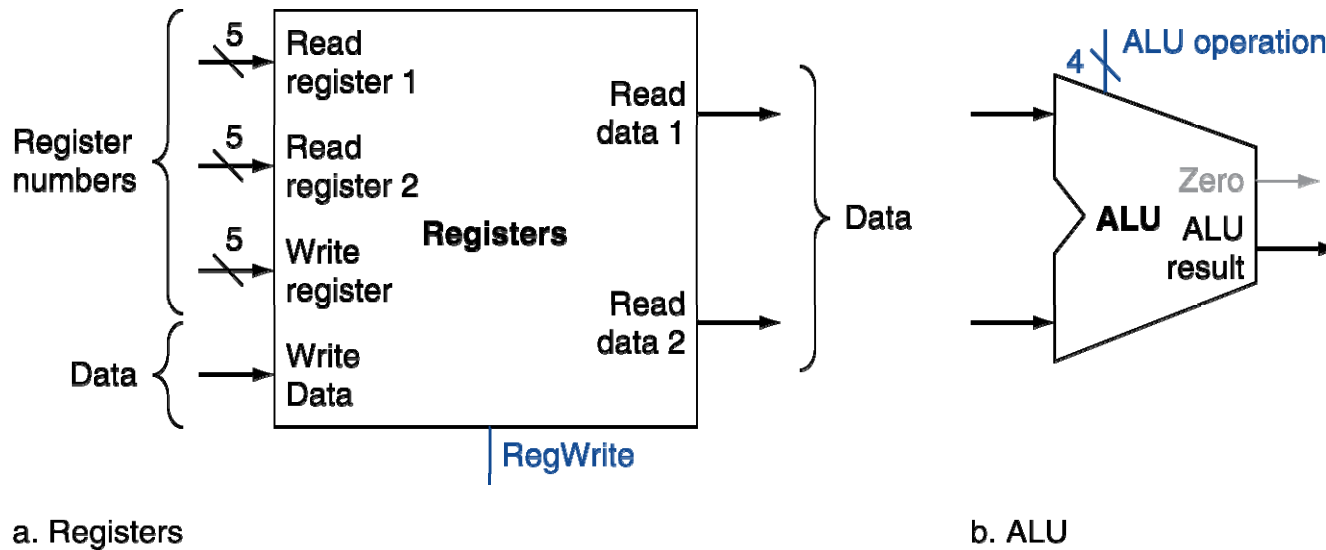- Write to register file
  - 1 input to the register file specifying the number
    - 5 bit wide inputs for the 32 registers
  - 1 input to the register file with the value to be written
    - 32 bit wide
  - Only for some instructions. RegWrite control signal.





## ■ ALU


- Takes two 32 bit input and produces a 32 bit output
- Also, sets one-bit signal if the results is 0
- The operation done by ALU is controlled by a 4 bit control signal input. This is set according to the instruction

# Data transfer instructions


- `lw $t1, offset_value($t2)`
- Load: Read memory and update register
  
- `sw $t1, offset_value($t2)`
- Store: Write register value to memory
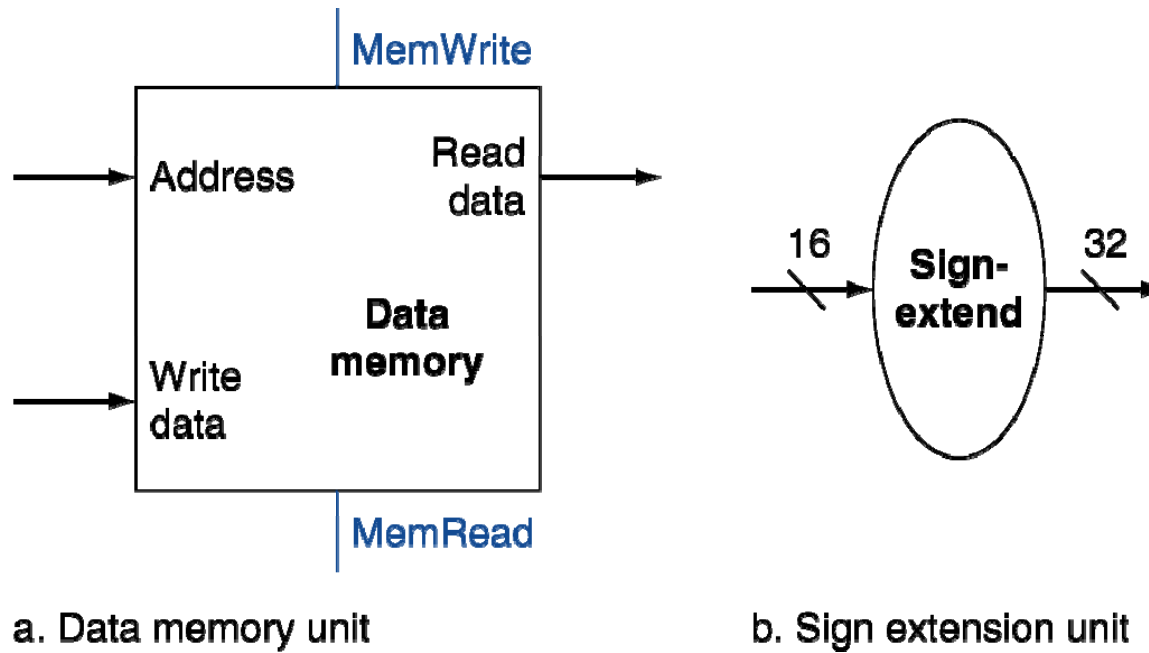
# Data transfer instructions


- Compute the memory address by adding the value in base register and the 16 bit offset
  - need the ALU
  - Calculate address using 16-bit offset
    - Use ALU, but sign-extend offset
- Write to or read from register
  - need the register file



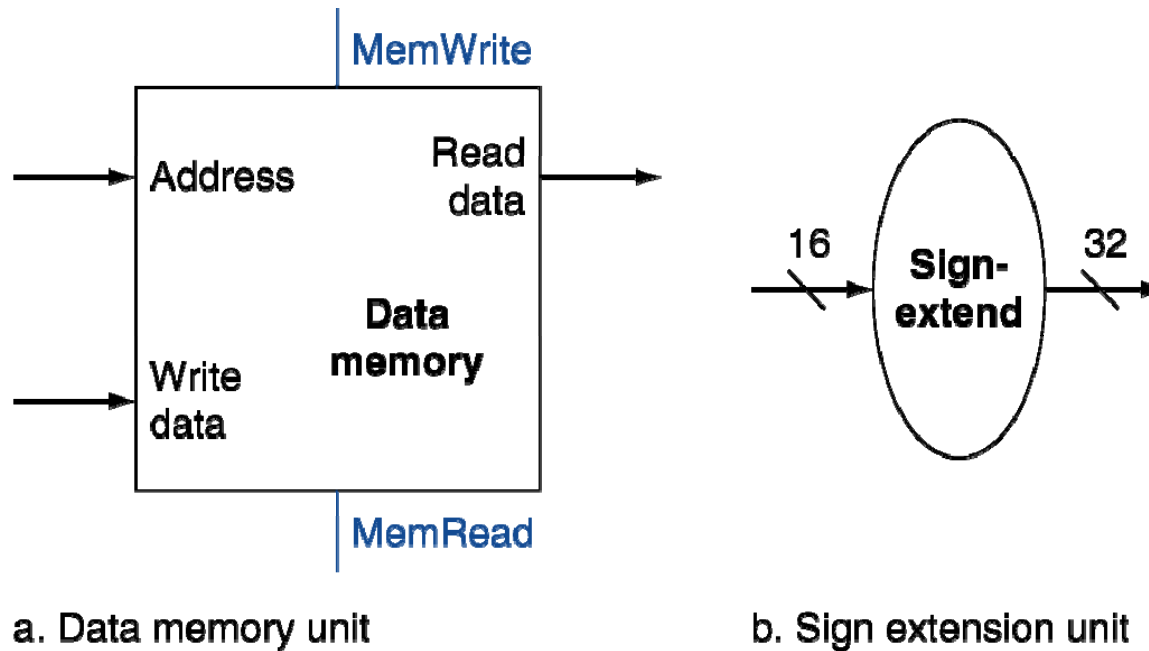- Two additional units – data memory and sign unit extension
- Data memory
  - State element with
    - input for address and data to be written
    - output for read result




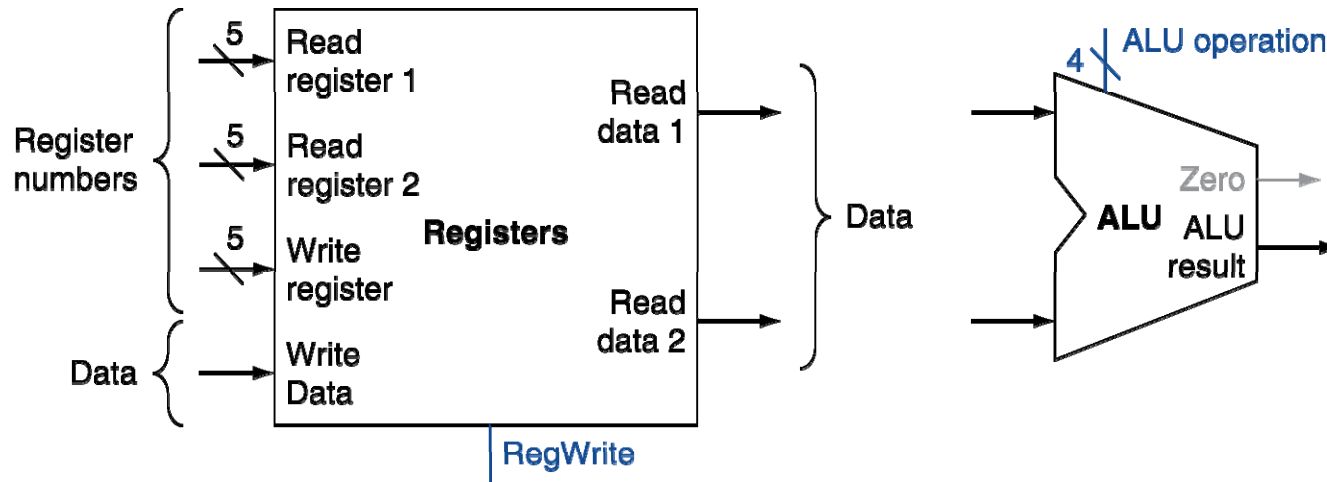- Data memory
  - Separate control for read and write
  - Control for read is required because reading from invalid address can lead to problems
- Sign-extension unit takes a 16 bit input and extend it to a 32 bit output



a. Registers

b. ALU

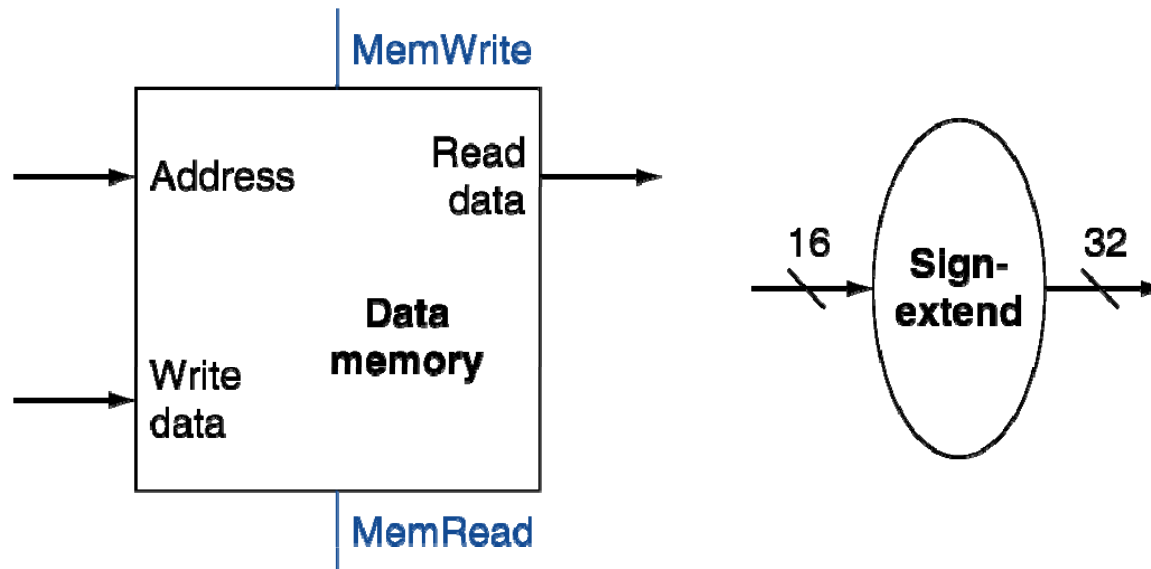

a. Data memory unit

b. Sign extension unit

# Composing the Elements for R-type and data transfer instructions

- A simple data path that does an instruction in one clock cycle
  - Each datapath element can only do one function at a time
  - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions

# Multiplexors


- An ALU might need input from
  - Two registers
  - Or one registers and one immediate field (or offset)
- To choose correctly from multiple sources, a hardware element called multiplexor is used with appropriate control signals



# Multiplexors

- The data written to registers may come from
  - Data memory
  - Or ALU
- To choose correctly from multiple sources, a hardware element called multiplexor is used with appropriate control signals

# R-Type/Load/Store Datapath

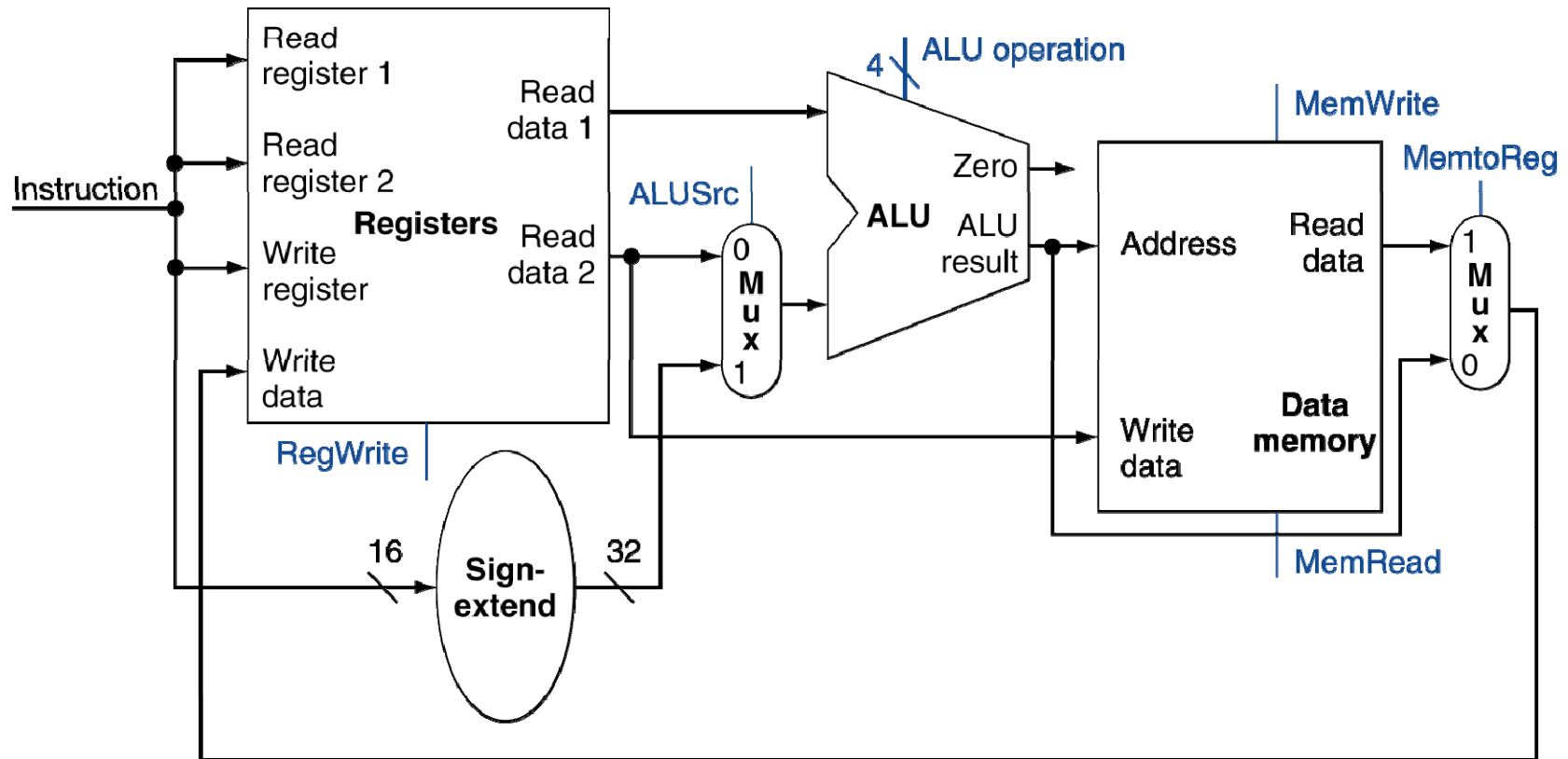


# Branch Instructions

- `beq $t1, $t2, offset`
- Read two registers and compare them
- Take the 16 bit offset and add it to the address of next instruction following the branch instruction to obtain the branch target address

# Branch Instructions

- Read register operands
- Compare operands
  - Use ALU, subtract and check Zero output
- Calculate target address
  - Sign-extend the offset
  - Shift left 2 places (word displacement)
  - Add to PC + 4
    - Already calculated by instruction fetch


# Branch Instructions

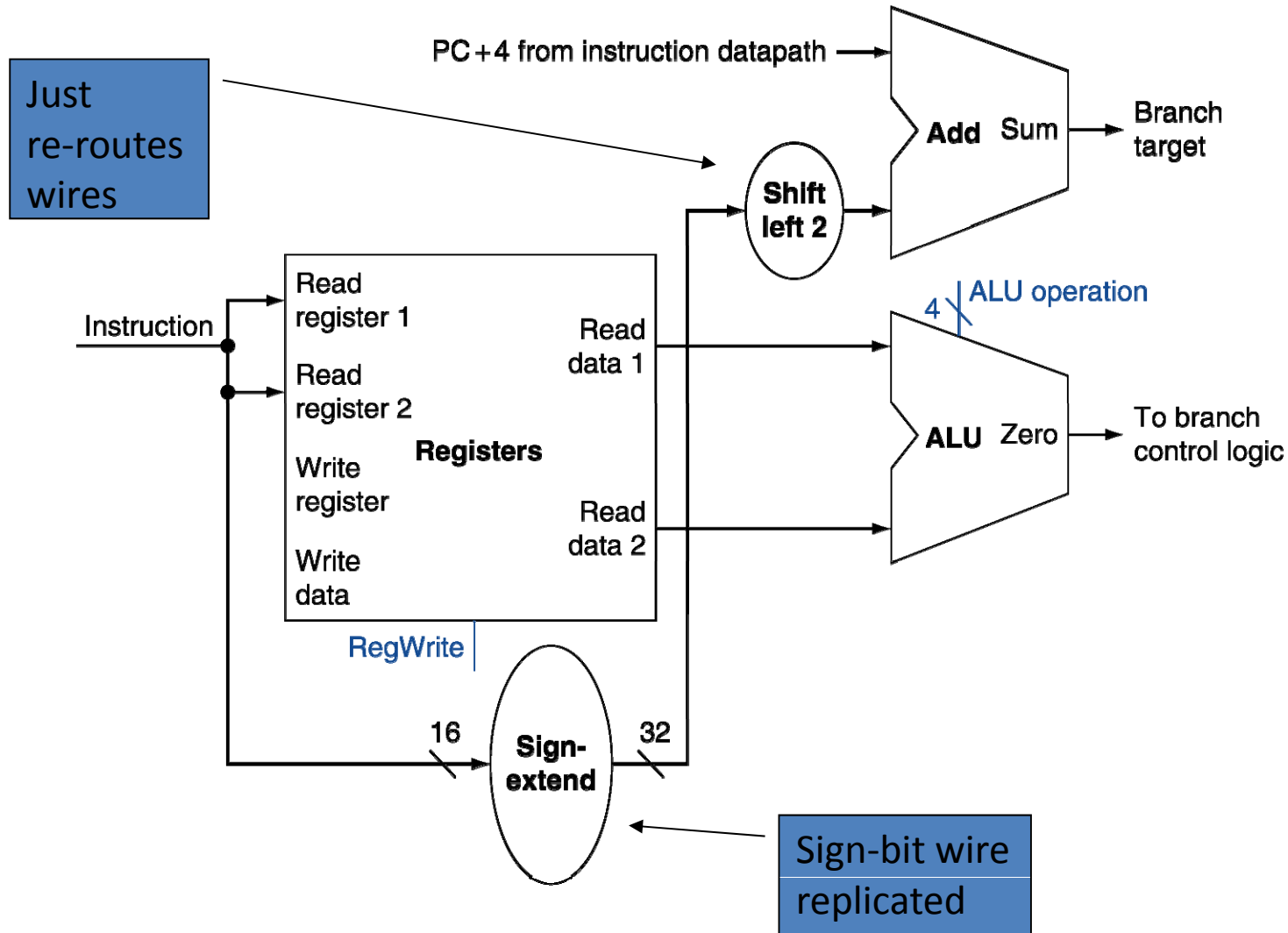


# Composing all elements together

- Instruction fetch datapath
- Datapath for R-type and memory instructions
- Datapath for branches
  
- Need an additional multiplexor to select the sequential address after branch or the branch target address to be written to the PC

# Datapath portion for Instruction Fetch

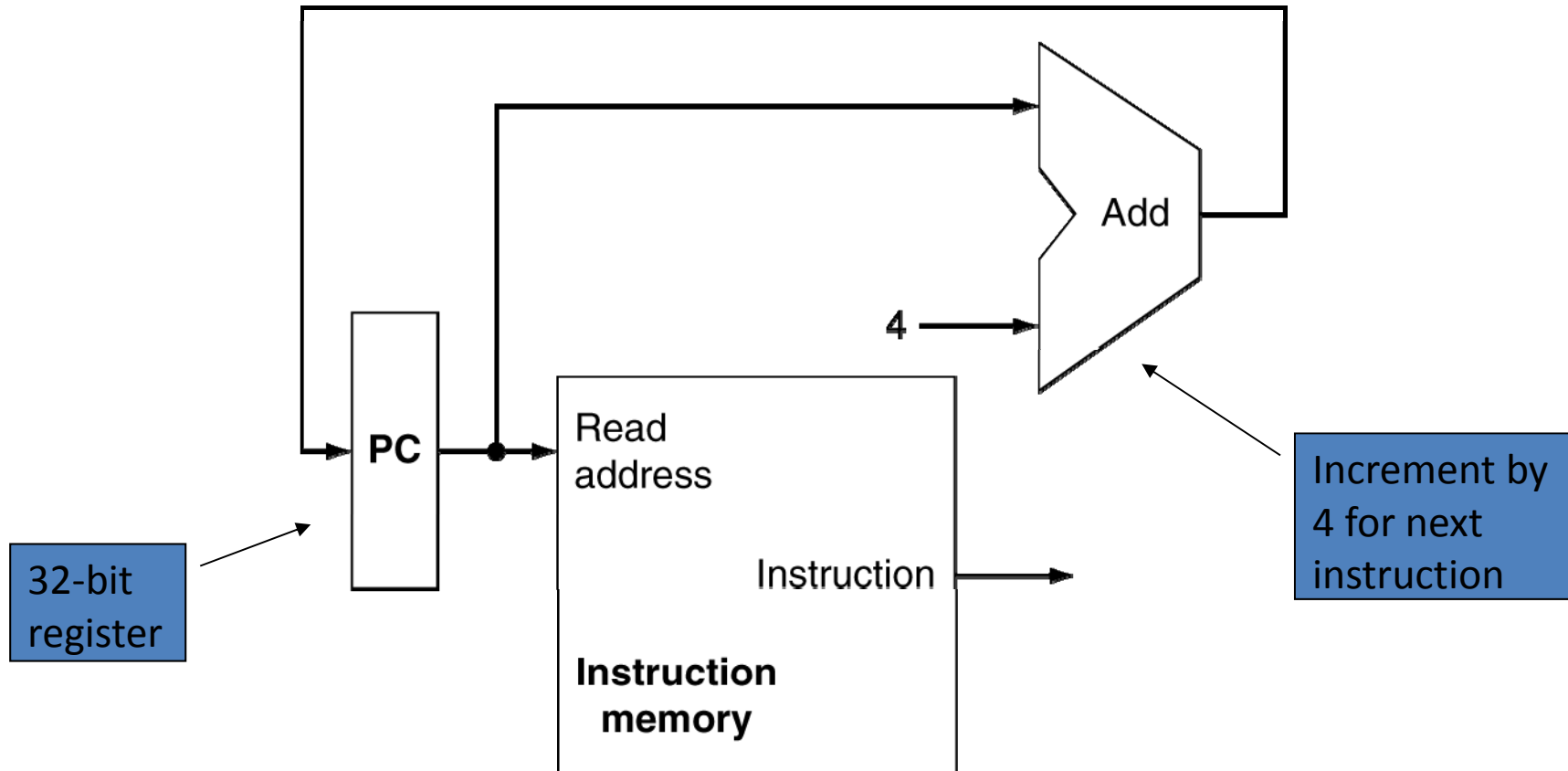


# Full Datapath

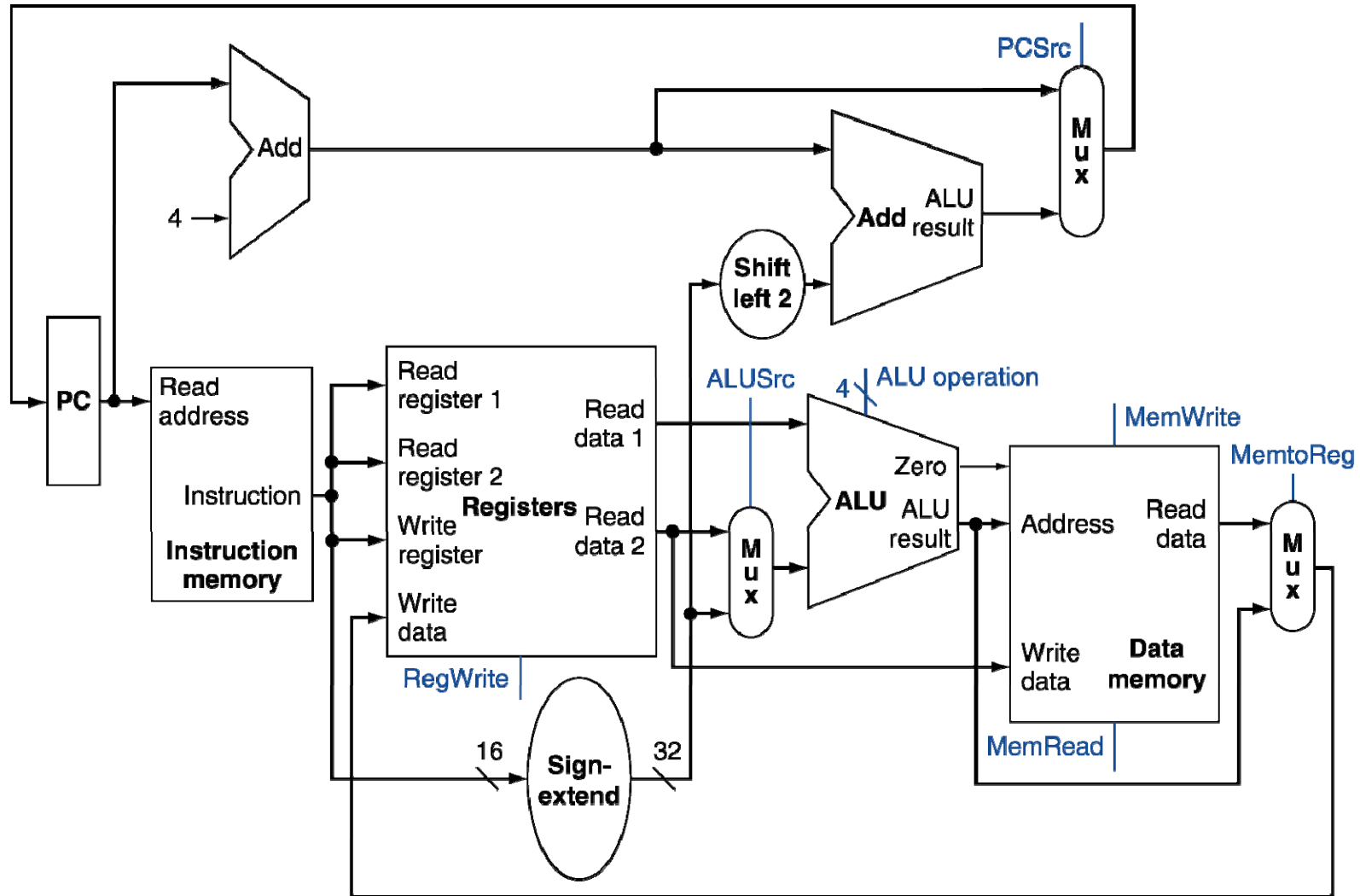




# Datapath With Control

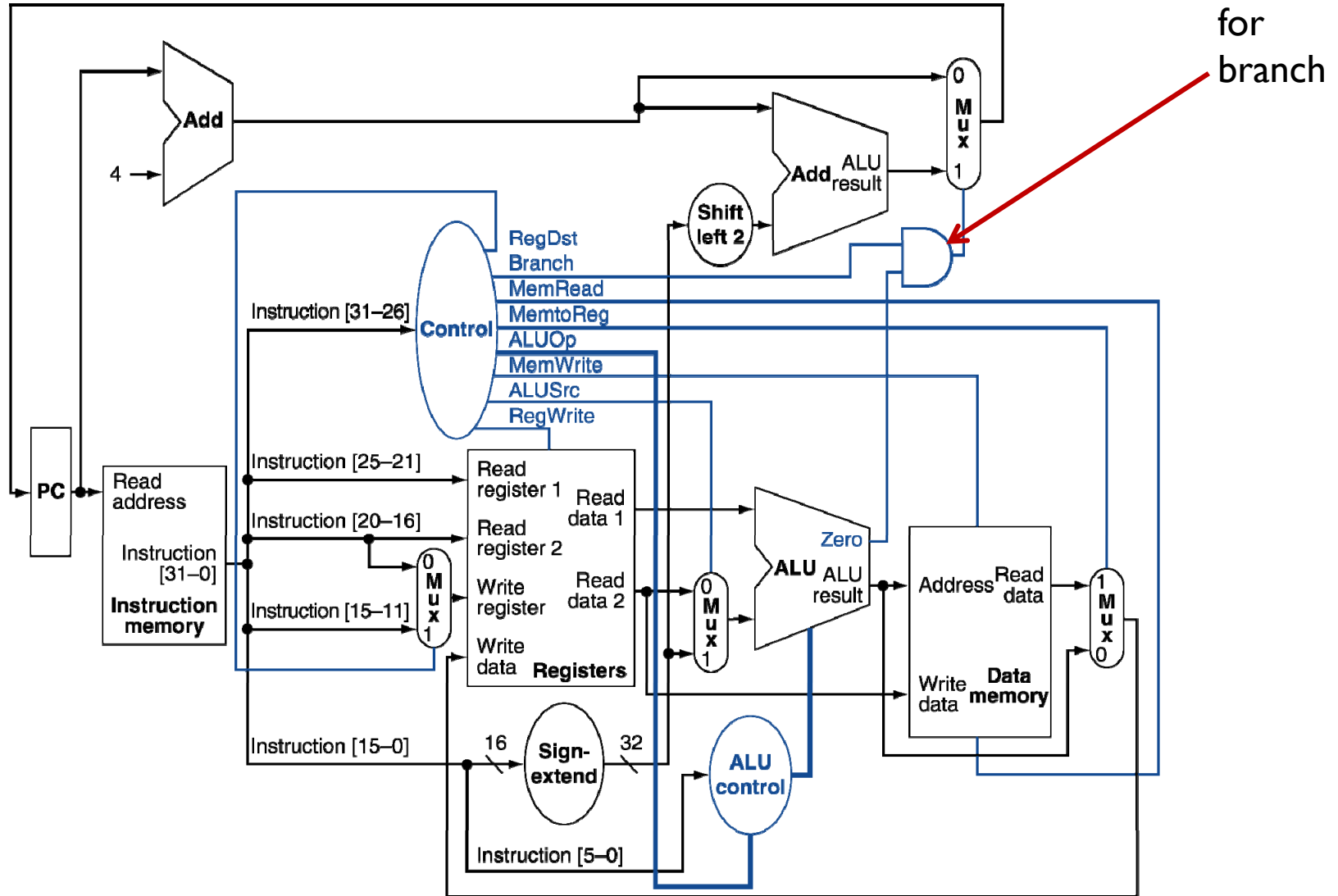

# A Recap: Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Adder

- $Y = A + B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 

- Arithmetic/Logic Unit

- $Y = F(A, B)$

 


# A Recap: State Elements

- Registers
  - Data Memory
  - Instruction Memory
- 
- Clocks are needed to decide when an element that contains state should be updated

# Recap from Lecture 1: CPU Clocking


- Operation of digital hardware governed by a constant-rate clock
- Clock period: duration of a clock cycle
- Clock frequency (rate): cycles per second

# Clocks

 

- A clock is a signal with a fixed cycle time (period)
- The clock frequency is the inverse of the cycle time

# Clocks

 



- The clock cycle time or clock period is divided into two portions:
  - when the clock is high
  - when the clock is low

# Clocking Methodology

- We study
  - Edge triggered methodology
    - Because it is simple
- Edge triggered methodology:
  - All state changes occur on a clock edge
  
# Clocking Methodology : State Elements



- Register: stores data in a circuit
  - Uses a clock signal to determine when to update the stored value
  - Edge-triggered: update when Clk changes from 0 to 1





  
# Clocking Methodology : State Elements

- Register with write control
  - Only updates on clock edge when write control input is 1
  - Used when stored value is required later



 
# Clocking Methodology

- Combinational logic transforms data during clock cycles
  - Between clock edges
  - Input from state elements, output to state element
    - The state elements, whose outputs change only after the clock edge, provide valid inputs to the combinational logic block.



 
# Clocking Methodology

- To ensure that the values written into the state elements on the active clock edge are valid, the clock must have a long enough period so that all the signals in the combinational logic block stabilize, then the clock edge samples those values for storage in the state elements.
- This constraint sets a lower bound on the length of the clock period, which must be long enough for all state element inputs to be valid.
- Longest delay determines clock period



It is possible to have a state element that is used as both an input and output to the same combinational logic block

 Ensure that the clock period is long enough



# Single Clock Cycle

- We studied a simple implementation where a single clock cycle is required for every instruction. Every instruction begins on one clock edge and completes execution on the next

# Performance Issues

- Longest delay determines clock period
  - Critical path: load instruction
  - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- The clock cycle must be extended to accommodate the longest instruction
- Improve performance by pipelining

# Conclusion

- ISA influences the design of datapath and control for a processor
- We studied an implementation based on single cycle